

Circuits from the Lab® Reference Designs

Circuits from the Lab® reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0410.

Devices Connected/Referenced	
AD5686A	Serial-Input, Voltage Output, Unbuffered 16-Bit DAC
ADA4500-2	Rail-to-Rail Input/Output, Zero Input Crossover Distortion Amplifier
ADR4520	Ultralow Noise, High Accuracy, 2.048 V Voltage Reference
LTC6820	Isolated SPI Communication Interface
ADP7112	20 V, 200 mA Linear Regulator

Programmable, 3-Channel LED Current Source Driver with isoSPI Repeater

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

[CN-0410 Circuit Evaluation Board \(EVAL-CN0410-ARDZ\)](#)

[ADICUP3029 \(EVAL-ADICUP3029\)](#)

Design and Integration Files

[Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 is a 3-channel, programmable, LED current driver with digital communications repeater capabilities.

Each of the three output channels is controlled by a single digital-to-analog converter (DAC), which simplifies the digital communications and reduces cost. Each channel can be individually programmed and is capable of sourcing 1 A of current through its load. The circuit also has an isoSPI™ repeater that allows multiple boards to be controlled with a single master. The repeater translates the serial port interface (SPI) signals into pulses that are transmitted through a twisted pair of wire and converted back to an SPI signal at the other end.

This solution is ideal for precision lighting control applications where a compact, scalable, single-supply, and highly linear, 3-channel, 16-bit buffered current source is required.

Rev. 0

Circuits from the Lab reference designs from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

One Technology Way, P.O. Box 9106, Norwood, MA 02062-9106, U.S.A.
Tel: 781.329.4700 www.analog.com
Fax: 781.461.3113 ©2018 Analog Devices, Inc. All rights reserved.

 


Figure 1. Linear 16-Bit Buffered Triple Output Voltage Output DAC (Simplified Schematic, All Connections and Decoupling Not Shown)

CIRCUIT DESCRIPTION

Digital-to-Analog Converter Output

Figure 1 shows the single-supply signal chain that consists of a voltage reference, a DAC, a DAC buffer, voltage to current conversion stage, and an isolated SPI communication interface.

The DAC is the [AD5686](#), a low power, quad, 16-bit, buffered voltage output DAC. The output voltage of the DAC is dependent on the reference voltage, as shown in the following equation:

$$V_{OUT} = \frac{V_{REF} \times D}{2^N}$$

where

D is the decimal data word loaded in the DAC register.

N is the number of bits.

For a reference of 2.048 V, and $N = 16$, the equation simplifies to the following:

$$V_{OUT} = (2.048 \times D) / 65536$$

This equation gives a V_{OUT} of 1.024 V at mid scale, and 2.048 V at full scale.

The LSB size is $2.048 \text{ V} / 65,536 = 31.25 \mu\text{V}$.

One LSB at 16 bits is also 0.0015% of full scale or 15 ppm of full scale.

The DAC reference pin is driven by a 2.0248 V reference device, the [ADR4520B](#). The [ADR4520B](#) voltage reference provides a

high precision, low noise (1 μV p-p, 0.1 Hz to 10 Hz) and stable reference to the DAC. The [ADR4520B](#) uses an innovative core topology to achieve high accuracy, temperature stability, and noise performance. The low output voltage temperature coefficient (2 ppm/°C maximum) and low long-term output voltage drift of the device also improve system accuracy over time and temperature variations. The initial room temperature accuracy of the [ADR4520B](#) is $\pm 0.02\%$ maximum, which is approximately 13 LSBs at 16 bits.

Voltage to Current Conversion

The [ADA4500-2](#) is selected as the operational amplifier. This device is a high precision amplifier with a maximum offset voltage of 120 μV , offset drift of less than 5.5 $\mu\text{V}/^\circ\text{C}$, 0.1 Hz to 10 Hz noise of 2 μV p-p, and maximum input bias current of 2 pA. Its key feature of rail-to-rail input and output swing with zero crossover distortion makes the [ADA4500-2](#) a suitable candidate for this function.

A typical rail-to-rail input amplifier uses two differential pairs to achieve rail-to-rail input swing (see the [MT-035 Tutorial](#)). One differential pair is active at the higher range of the input common-mode voltage, and the other pair is active at the lower end. This classic dual differential pair topology introduces crossover distortion during the handoff of one differential pair to the other. The change in offset voltage causes nonlinearity when the amplifier is used as a DAC buffer. The [ADA4500-2](#) uses an integrated charge pump in its input structure to achieve

rail-to-rail input swing without the need for a second differential pair. Therefore, it does not exhibit crossover distortion. Using a zero crossover distortion amplifier in this single-supply system provides wide dynamic output range while maintaining linearity over the input common mode/input digital code range. Details of the operation of the [ADA4500-2](#) can be found in the [ADA4500-2](#) data sheet.

The [ADA4500-2](#) is a suitable candidate with high input impedance, 2 pA maximum input bias current at room temperature, and 190 pA maximum input bias current over temperature. This low bias current results in 1.2 μ V of worst-case error due to input bias current, which is much less than 1 LSB.

The output the DAC is buffered and used to turn on the MOSFET, with feedback taken from the current sense resistor. A current source must be compensated properly to prevent oscillations when driving an inductive load such as the wiring to the LED board. The R_x resistor, R_y resistor, C_x capacitor, and C_y output capacitor provide frequency compensation. This circuit tolerates a load inductance of up to 5 μ H. (For example, an LED board wired to the [CN-0410](#), located 5 m away, with 16-gauge wire, spaced 10 mm apart, is approximately 5.5 μ H. Most practical installations have conductors much closer together, and therefore lower inductance.) An [LTspice](#)® simulation is provided to aid in compensating for other loads.

 


Figure 2. Voltage to Current Stage

The circuit in Figure 2 converts the control voltage from the DAC into a current that drives the LED. The MOSFET in the circuit is able to handle currents of up to 6.3 A. However, the current is limited to 1 A, which is the maximum rated current of the LED.

The maximum current is limited by the resistors on each channel: R_7 , R_{14} , and R_{21} . The maximum current can be calculated by

$$I_{MAX} = 2.048 \text{ V} / R (\Omega) = 1.024 \text{ A}$$

where $R = 2 \Omega$.

Power Dissipation and Thermal Considerations

When driving LEDs with a linear current source, the power dissipation of the sense resistors and MOSFETs must be considered. Power dissipation in the sense resistors is always less than their 3 W rating, even at the maximum setpoint current of 1 A. MOSFET power dissipation increases if the LED supply voltage is increased, resulting in more voltage drop across the MOSFET. When used with the [CFTL-LED-BAR](#) and a supply voltage of 16 V, keeping below half scale (500 mA) reduces dissipation. Under these conditions, the board temperature reaches approximately 79°C in the vicinity of the MOSFETs with the board positioned vertically in still air. The [LTspice](#) simulation can also be used to estimate power dissipation for other load conditions.

For higher power levels, a heat sink or forced convective cooling (fan) may be required to keep the board temperature lower than 130°C, the recommended maximum for FR-4. Figure 3 shows the board operating in free air, at half of its maximum power on Channel A at 500 mA, with an input voltage of 16 V.

The resistors reach 95°C, and the area around the FETs is approximately 79°C.

 


Figure 3. Board Temperature at 500 mA

The board has an area where there is no copper pour (shown in Figure 4), which acts as a thermal isolation barrier from the rest of the circuit. This area can be seen in Figure 3, where there is a drastic drop in temperature across the two ground planes. This barrier helps keep the temperature drift due to the components on the left side of the board to its minimum.

 


Figure 4. Ground Layer—Thermal Barrier

Isolated Daisy-Chained SPI Control

The circuit also has a SPI communications protocol repeater, which is enabled by the [LTC6820](#). This device enables multiple boards to be connected to a single twisted pair cable with only one master controlling the whole chain.

The [LTC6820](#) provides bidirectional SPI communications between two isolated devices through a single twisted pair connection. Each [LTC6820](#) encodes logic states into signals that are transmitted across an isolation barrier to another [LTC6820](#).

The receiving [LTC6820](#) decodes the transmission and drives the slave bus to the appropriate logic states. The isolation barrier is bridged by a simple pulse transformer to achieve basic isolation on the [CN-0410](#). With layout optimization, an isolation voltage of 1500 V can be achieved, limited by the transformer. Refer to the [LTC6820](#) for other recommended transformers.

The [LTC6820](#) drives differential signals using matched source and sink currents, eliminating the requirement for a transformer center tap and reducing electromagnetic interference (EMI). Precision window comparators in the receiver detect the differential signals.

The drive currents and the comparator thresholds are set by a simple external resistor divider, allowing the system to be optimized for required cable lengths and desired signal-to-noise performance.

Integral Nonlinearity (INL) and Differential Nonlinearity (DNL) Measurements

Measured results show that the combination of the [AD5686](#), [ADR4520B](#), and [ADA4500-2](#) is an excellent solution for high accuracy, low noise performance applications. The [ADA4500-2](#) maintains the linearity of the DAC with no crossover distortion.

INL error is the deviation in LSB of the actual DAC transfer function from an idealized transfer function. DNL error is the difference between an actual step size and the ideal value of 1 LSB. This system solution provides a 16-bit resolution with ± 1 LSB DNL and INL. Figure 5 and Figure 6 show the DNL and INL performance of the circuit.

 


Figure 5. Differential Nonlinearity (DNL)

 


Figure 6. Integral Nonlinearity (INL)

Note that the DNL and INL measurements exclude the 100 codes (approximately 4 mV) from the lower end of the range, because the rail-to-rail output stage becomes nonlinear over this region, as described in [MT-035 Tutorial](#).

Noise Measurements

The targeted 0.1 Hz to 10 Hz noise for the whole board is to be less than 24 μV p-p. The [AD5686](#), [ADA4500-2](#), and [ADR4520B](#) contribute a calculated total of 9 μV p-p to the whole circuit. The true noise of the circuit is measured by using a noise measuring box with a gain of 10,000 and filtered between 0.1 Hz and 10 Hz.

It is advised to take the cleanest supply when taking the noise measurements. Therefore, the [ADICUP3029](#) was removed from the setup, and the supply is taken from a 9 V battery.

 


Figure 7. Test Setup for Measuring 0.1 Hz to 10 Hz Noise with Gain of 10,000

The noise of the box itself and the circuit with the noise box were measured, and their noises are 4.22 μV p-p and 8.38 μV p-p, respectively. Uncorrelated, Gaussian noise sources add in a root sum square (RSS) manner. Therefore, the noise of the [CN-0410](#) is

$$\text{True Noise} = \sqrt{(Y_{\text{uVp}} - p)^2 - (X_{\text{uVp}} - p)^2}$$

Using this equation, the true noise of the circuit is calculated to be 7.23 μV p-p.

Board Layout Considerations

It is important to carefully consider the power supply and ground return layout on the board. It is recommended that the printed circuit board (PCB) have separate analog and digital sections. If the circuit is used in a system where multiple devices require an analog ground to digital ground connection, make the connection at only one point. Bypass all power supply pins with at least 0.1 μF capacitors. Place these bypass capacitors as physically close as possible to the device, with the capacitor ideally right up against the device. Choose the 0.1 μF capacitor to have low effective series resistance (ESR) and low effective series inductance (ESL), such as ceramic capacitors. This 0.1 μF capacitor provides a low impedance path to ground for transient currents. Use large traces for the power supply lines to provide a low impedance supply path. Use proper layout, grounding, and decoupling techniques to achieve optimum performance (see the [MT-031 Tutorial, Grounding Data Converters and Solving the Mystery of AGND and DGND](#) and [MT-101 Tutorial, Decoupling Techniques](#)).

The AD5686 is available in 16-lead LFCSP or 16-lead TSSOP packages. The [ADR4520](#) is available in an 8-lead SOIC package, and the [ADA4500-2](#) is available in 8-lead MSOP or 8-lead LFCSP packages.

COMMON VARIATIONS

For a lower power consumption solution (at lower speed), use the [ADA4505-1/ADA4505-2/ADA4505-4](#) as the output buffer. The [ADA4505](#) family is a micropower, zero-crossover distortion amplifier with low input bias current.

The [ADR420](#), [ADR430](#), and [ADR440](#) are suitable candidates to provide the 2.048 V reference. These devices feature high accuracy, low noise, and accept input voltages of up to 18 V.

For a lower power DAC, the [AD5064](#) is a quad-channel DAC with lower power consumption than the [AD5686](#).

CIRCUIT EVALUATION AND TEST

This circuit uses the [EVAL-CN0410-ARDZ](#) circuit board, the [CFTL-LED-BAR](#), and the [EVAL-ADICUP3029](#). The [EVAL-CN0410-ARDZ](#) is stacked on top of the [EVAL-ADICUP3029](#) using the Arduino-compatible pins

Equipment Needed

- PC with a USB port and Windows® 7 or above
- [EVAL-CN0410-ARDZ](#) circuit evaluation board
- [CFTL-LED-BAR](#) evaluation board
- [ADICUP3029](#) evaluation platform or equivalent interface
- [CrossCore Embedded Studios \(IDE\)](#)
- Power supply: 9 V to 19.2 V wall wart

Getting Started

Load the sample code onto the [CrossCore Embedded Studios IDE](#) by following the instructions in the [Quick Start User Guide](#).

Functional Block Diagram

Figure 8 shows the functional block diagram of the test setup.

 


Figure 8. Test Setup Functional Block Diagram

Setup

Connect the [EVAL-CN0410-ARDZ](#) by mounting it on top of the [EVAL-ADICUP3029](#) board using the Arduino-compatible headers with their corresponding headers, as shown in Table 1.

Table 1. Connection Between [EVAL-CN0410-ARDZ](#) and [ADICUP3029](#) Boards

EVAL-CN0410-ARDZ	ADICUP3029
DIGI 1	P6
DIGI 0	P7
POWER	P4
ANALOG	P3

Table 2. Connection Between [EVAL-CN0410-ARDZ](#) and [CFTL-LED-BAR](#) Boards

CN-0410 Connector	CFTL-LED-BAR Connector
P1.1	P1.2
P1.2	P1.1
P6.1	P5.2
P6.2	P5.1
P9.1	P9.2
P9.2	P9.1

Then connect the USB cable from the debug port of the [EVAL-ADICUP3029](#) to the USB port of the PC.

Test

With the sample code built and loaded onto the [EVAL-ADICUP3029](#), and the [EVAL-CN0410-ARDZ](#) mounted on top with the [CFTL-LED-BAR](#) connected, the device communicates with the PC, and codes can now be written to the device via the UART. The circuit can be tested by varying the code written to the board to alter the intensity of the LEDs.

For complete information and details regarding test setup and how to use the software and hardware combined, refer to the [CN-0410 User Guide](#).

More information regarding the [EVAL-ADICUP3029](#) board is available in the [EVAL-ADICUP3029 User Guide](#).



Figure 9. [EVAL-CN0410-ARDZ](#) Evaluation System

LEARN MORE

Kester, Walt. *The Data Conversion Handbook*, Chapter 3 and Chapter 7, Analog Devices. 2005.

MT-015 Tutorial, *Basic DAC Architectures II: Binary DACs*, Analog Devices.

MT-016 Tutorial, *Basic DAC Architectures III: Segmented DACs*, Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of AGND and DGND*, Analog Devices.

MT-035 Tutorial, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

Data Sheets and Evaluation Boards

[AD5686A Data Sheet](#)

[ADA4500-2 Data Sheet](#)

[ADR4520 Data Sheet](#)

[LTC6820 Data Sheet](#)

[ADP7112 Data Sheet](#)

REVISION HISTORY

6/2018—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab reference designs are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab reference designs in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab reference designs. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab reference designs are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab reference designs at any time without notice but is under no obligation to do so.

©2018 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.
CN16045-0-6/18(0)

