Search

Introduction
Specification
Dimension
Pinout
User Guide
Application Sample (RGB LED Ring - 12)
Project 1: Dazzling Neon Light
Project 2: LED Ring Cascade
Project 3: LED Ring Clock
Project 4: LED Ring Compass
Project 5: Rainbow Breathing LED Ring
Project 6: Color Palette
2. Makecode Programming
User Guide
FAQ
More Documents

SKU:DFR0888

Introduction

Specification

Shine like You
With 12 RGB LED
Beads, this
Gravity: I2C
LED Ring is a
cool appearance
touch for a great partner for your interactive
projects. Each LED bead can be addressed individually
and combined with any other LED beads to create
vivid animations. It could turn into a compass that tells
you the direction, a rainbow breathing light, or even a
colorful decoration for robots. Its I2C interface makes it
easy to play with this colorful RGB LED ring by cascading it.

- Supply voltage: 3.3~5V
- Interface type: I2C x1
- Interface function: cascade multiple lamp rings through I2C

Dimension

Pinout

Num	Label	Description
1	SCL	Digital input port
2	+	VCC
3	SDA	Digital input port
4	-	GND

Note: For the reference of the port, RX and DAT represents input and output terminals respectively.

1. Mind+ Programming

User Guide

The cascading feature of the RGB LED contained needs to be added before using the RGB LED. Click "Extension" at the bottom left corner of the Mind+ interface, search for "WS2812 RGB LED" in the "Display" menu bar and click it to add. Then you can find the RGB LED module in the "Actuator" menu bar.

Application Sample (RGB LED Ring - 12)

Project 1: Dazzling Neon Light

Project Introduction

Display color gradients of the 12 RGB LEDs to create a cool neon light effect. Click and drag out the following code blocks in the script area.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 12 LED Beads x 1

Hardware Connection

Program Screenshot

Project 2: LED Ring Cascade

Related to cascade LED ring

Click and drag out the following code blocks to create a cascade LED ring effect. Each LED bead will be lit up from the first to the last one in order.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 12 LED Beads x 1
- RGB LED Ring - 24 LED Beads x 1
- RGB LED Ring - 60 LED Beads x 1
- Pin-to-Pin JST Cable x 1

Hardware Connection

Program Screenshot

Note: When using the cascaded lamp ring, the power supply must be connected to the external power supply, and not received by using a USB or external power supply.

Product Introduction

To achieve a dazzling neon light effect similar to project 1 by cascading three types of LED rings.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 12 LED Beads x 1
- RGB LED Ring - 24 LED Beads x 1
- RGB LED Ring - 60 LED Beads x 1
- Pin-to-Pin JST Cable x 3

Hardware Connection

Program Screenshot

Project 3: LED Ring Clock

Product Introduction

Clocks are a must-have in our daily routine. The most general clocks are electronic and quartz clocks. In this case, we will be evolved by using a 12-bit universal ring.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 12 LED Beads x 1
- RGB LED Ring - 24 LED Beads x 1

Hardware Connection

Program Screenshot

Application Sample (RGB LED Ring - 24)

Project 4: LED Ring Compass

Project Introduction

Compass is commonly used to tell the direction, and nowadays it is usually integrated with a variety of sensors. Here, we use software to help us determine the North. First based on the magnetic sensor data, then the corresponding LED will be lit up to indicate the direction of the compass.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 24 LED Beads x 1

Hardware Connection

Program Screenshot

Project 5: Rainbow Breathing LED Ring

Project Introduction

Rainbow breathing light is the light controlled to gradually change from dark to bright and then from bright to dark, and the color is changing at the same time. We will employ the RGB LED ring to make a rainbow breathing ring flowing your eyes.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 12 LED Beads x 1

Hardware Connection

Program Screenshot

Project 6: Color Palette

Project Introduction

We are all familiar with RGB and know that mixing that with different brightness of red, green and blue light will form the principle of getting 16 million different colors by varying their colors but the RGB ring serve as our color palette and mix the three basic colors of light.

Hardware Preparation

- micro:bit x 1
- I2C expansion Board x 1
- RGB LED Ring - 12 LED Beads x 1
- Rotary Potentio Sensor x 3

Hardware Connection

Program Screenshot

2. Makecode Programming

User Guide

Click the extensions in Mind Code and add the lamp strip library into the extensions.

FAQ